

DAY-85

#100DAYSOFRTL

AIM:--- IMPLEMENTATION OF CLOCK BUFFER.


VERILOG CODE:--

```
1 module clock_buffer(mclk,bclk);  
2 input mclk;  
3 output bclk;  
4 buf b1(bclk,mclk);  
5 endmodule
```

TESTBENCH CODE:---

```
1 module clock_buffer_tb();
2 reg mclk;
3 wire bclk;
4 realtime t1,t2,t3,t4,t5,t6;
5 parameter T=10;
6 clock_buffer dut(mclk,bclk);
7 initial
8 begin
9     mclk=1'b0;
10    forever #(T/2) mclk=~mclk;
11 end
12 task master;
13 begin
14     @(posedge mclk) t1=$realtime;
15     @(posedge mclk) t2=$realtime;
16     t3=t2-t1;
17 end
18 endtask
19
20 task bufout;
21 begin
22     @(posedge bclk) t4=$realtime;
23     @(posedge bclk) t5=$realtime;
24     t6=t5-t4;
25 end
26 endtask
27
28 task freq_phase;
29 realtime f,p;
30 begin
31     f=t6-t3;
```

WAVEFORM:-----

 

SCHEMATIC BLOCK :-----

