 


DAY-94

#100DAYSOFRTL

AIM:--- IMPLEMENTATION OF FINITE STATE MACHINE



VERILOG CODE:--

```

module top_module(
    input clk,
    input areset,
    input j,
    input k,
    output out);

    parameter OFF=0, ON=1;
    reg state, next_state;


    always @(*) begin
        if(state==OFF&&j==0)
            next_state<=OFF;
        else if(state==OFF&&j==1)
            next_state<=ON;
        else if(state==ON&&k==1)
            next_state<=OFF;
        else if(state==ON&&k==0)
            next_state<=ON;
        else
            next_state<=next_state;
    end

    always @(posedge clk, posedge areset) begin
        if(areset)
            state<=OFF;
        else
            state<=next_state;
    end
    assign out = (state == OFF?0:1);
  
```

TESTBENCH CODE:---

```
1  timescale 1ns/1ps
2
3  module top_module_tb;
4
5      // Inputs
6      reg clk;
7      reg areset;
8      reg j;
9      reg k;
10
11     wire out;
12
13     top_module uut (
14         .clk(clk),
15         .areset(areset),
16         .j(j),
17         .k(k),
18         .out(out)
19     );
20
21     always begin
22     end
23
24     initial begin
25         clk = 0;
26         areset = 0;
27         j = 0;
28         k = 0;
29         #10 areset = 1;
30         #10 areset = 0;
```

WAVEFORM:-----

 

SCHEMATIC BLOCK :-----

