


DAY-24

#100DAYSOFRTL

PROBLEM STATEMENT:--

1. Implement the following

Implement the following circuit:

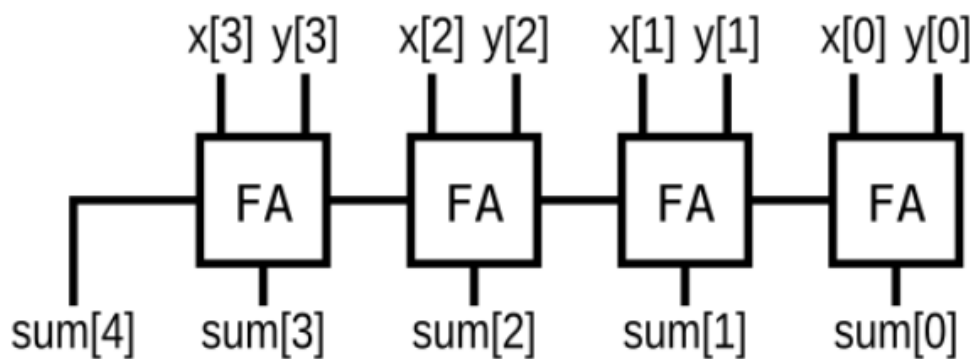

("FA" is a full adder)

Write your solution here

[Load a previous submission] ▾

Load

```
1 module top_module (
2     input [3:0] x,
3     input [3:0] y,
4     output [4:0] sum);
5
6     wire w1,w2,w3;
7
8     full_adder fa1(x[0],y[0],1'b0,w1,sum[0]);
9     full_adder fa2(x[1],y[1],w1,w2,sum[1]);
10    full_adder fa3(x[2],y[2],w2,w3,sum[2]);
11    full_adder fa4(x[3],y[3],w3,sum[4],sum[3]);
12
13 endmodule
14
15 module full_adder(input a,b,cin,output cout,sum);
16
17     assign sum=a^b^cin;
18     assign cout=a&b | b&cin | a&cin;
19
20 endmodule
```

exams/m2014_q4j — Compile and simulate

Running Quartus synthesis. [Show Quartus messages...](#)

Running ModelSim simulation. [Show Modelsim messages...](#)

Status: Success!

You have solved 58 problems. [See my progress...](#)