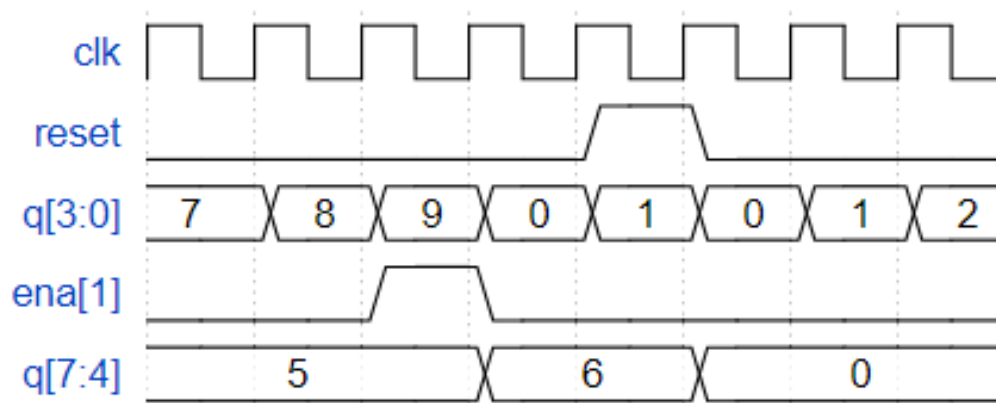


## DAY-67

### #100DAYSOFRTL

#### PROBLEM STATEMENT:--

1. Build a 4-digit BCD (binary-coded decimal) counter. Each decimal digit is encoded using 4 bits:  $q[3:0]$  is the ones digit,  $q[7:4]$  is the tens digit, etc. For digits  $[3:1]$ , also output an enable signal indicating when each of the upper three digits should be incremented.




```


1 module top_module (
2     input clk,
3     input reset,    // Synchronous active-high reset
4     output [3:1] ena,
5     output [15:0] q);
6 always @(posedge clk) begin
7     if(reset) begin
8         q = 0;
9         ena = 0;
10    end
11    else begin
12        q[3:0] = q[3:0] + 1;
13        ena[1] = (q[3:0] == 9) ? 1 : 0;
14        if(q[3:0] == 10) begin
15            q[3:0] = 0;
16            q[7:4] = q[7:4] + 1;
17        end
18        ena[2] = ((q[7:4] == 9) && (q[3:0] == 9)) ? 1 : 0;
19        if(q[7:4] == 10) begin
20            q[7:4] = 0;
21            q[11:8] = q[11:8] + 1; end
22        ena[3] = ((q[11:8] == 9) && (q[7:4] == 9) && (q[3:0] == 9)) ? 1 : 0;
23        if(q[11:8] == 10) begin
24            q[11:8] = 0;
25            q[15:12] = q[15:12] + 1;
26        end
27        if(q[15:12] == 10) begin
28            q = 0;
29        end
30    end
31 end
32 endmodule

```

#### 100 rollover

 

### Roll-over at count 90 and 100

 

## Status: Success!

You have solved 92 problems. [See my progress...](#)

### Timing diagrams for selected test cases

These are timing diagrams from some of the test cases we used. They may help you debug your circuit. The diagrams show inputs to the circuit, outputs from your circuit, and the expected reference outputs. The "Mismatch" trace shows which cycles your outputs don't match the reference outputs (0 = correct, 1 = incorrect).

#### Counting

