

DAY-21

#100DAYSOFRTL

PROBLEM STATEMENT:--

1. create a half adder. A half adder adds two bits (with no carry-in) and produces a sum and carry-out.

Write your solution here

Last non-success: 3/21/2024, 9:58:59 PM

Load

```
1 module top_module(  
2     input a, b,  
3     output cout, sum );  
4  
5     assign sum=a^b;  
6     assign cout=a&b;  
7  
8 endmodule  
9
```

Submit

Submit (new window)

Upload a source file... 

hadd — Compile and simulate

Running Quartus synthesis. [Show Quartus messages...](#)

Running ModelSim simulation. [Show Modelsim messages...](#)

Status: Success!

You have solved 55 problems. [See my progress...](#)