

DAY-32

#100DAYSOFRTL

PROBLEM STATEMENT:--

1. A single-output digital system with four inputs (a,b,c,d) generates a logic-1 when 2, 7, or 15 appears on the inputs, and a logic-0 when 0, 1, 4, 5, 6, 9, 10, 13, or 14 appears. The input conditions for the numbers 3, 8, 11, and 12 never occur in this system. For example, 7 corresponds to a,b,c,d being set to 0,1,1,1, respectively.

Determine the output out_sop in minimum SOP form, and the output out_pos in minimum POS form

Write your solution here

[Load a previous submission] ▾

Load

```
1 module top_module (  
2     input a,  
3     input b,  
4     input c,  
5     input d,  
6     output out_sop,  
7     output out_pos  
8 );  
9 assign out_sop = (c&d)|(~a&~b&c);  
10    assign out_pos = c&(~b|~c|d)&(~a|~c|d);  
11  
12 endmodule  
13
```

Submit

Submit (new window)

Upload a source file... ↕

exams/ece241_2013_q2 — Compile and simulate

Running Quartus synthesis. [Show Quartus messages...](#)

Running ModelSim simulation. [Show Modelsim messages...](#)

Status: Success!

You have solved 66 problems. [See my progress...](#)